

Series				
	R1	R2	R3	TOTAL
E	→			ADD
I	→			EQUAL
R	→			ADD
P	→			ADD
Parallel				
	R1	R2	R3	TOTAL
E	→			EQUAL
I	→			ADD
R	→			DIMINISH
P	→			ADD

$$E_{\text{total}} = E_1 + E_2 + E_3$$

$$R_{\text{total}} = R_1 + R_2 + R_3$$

$$P_{\text{total}} = P_1 + P_2 + P_3$$


$$I_{\text{total}} = I_1 = I_2 = I_3$$

$$E_{\text{total}} = E_1 = E_2 = E_3$$

$$I_{\text{total}} = I_1 + I_2 + I_3$$

$$R_{\text{total}} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

$$P_{\text{total}} = P_1 + P_2 + P_3$$

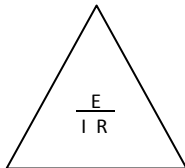

If you know E and I, and wish to determine R, just eliminate R from the picture and see what's left